

ECE 165 – Homework #4




Due: Never!
(but it is recommended to do the problems before the midterm)

Problem 1.

a) Calculate V_{out} for the pseudo-NMOS inverter when:

- $V_{in} = 0V$
- $V_{in} = V_{DD}$


Assume $\mu_n C_{ox} = 2 \mu_p C_{ox}$, $V_{DSAT,\{n,p\}} = 0.2V$, $V_{tn} = |V_{tp}| = 0.4V$, and $V_{DD} = 1.0V$. Ignore DIBL and channel-length modulation.

 

- Ignoring leakage, does this gate consume static power?
- Calculate the logical effort (i.e. g) of the gate. Remember that to calculate g , we compare to an inverter with the same current capability for a particular transition. Please use the class convention when sizing (i.e., keep the inverter P/N ratio 2/1).
- Would you ever use a gate like this? A brief explanation discussing the pros and cons is fine.

Problem 2.

 a) Calculate the input capacitance x , y , z that minimize the delay through the following circuit to V_{crit} . Note that in this problem, the input capacitance of each gate is proportional to the capacitance of a single NMOS transistor.



- What is the delay to V_{crit} and V_{other} in units of τ_{inv} ?
- Now resize the circuit for minimum delay to V_{other} and recalculate both delays

Problem 3.

- a) Design a single stage gate representing the function $F = \overline{(A + B)CD}$ using complementary static CMOS. Size the transistors for equal (worst case) rise/fall times.
- b) Draw a stick diagram layout, using shared and merged contacts as much as possible. Annotate your schematic with all parasitic diffusion capacitance. Please use colored pens/pencils (or at least clearly label all lines).
- c) Calculate the worst case pull up Elmore delay.